
Integrated Circuits and Systems

Zoran Stamenković

stamenkovic@ihp-microelectronics.com






International Organization for Migration (IOM)
Organisation internationale pour les migrations (OIM)
Organización Internacional para las Migraciones (OIM)



Topics

- **Analog Circuits**
 - Amplifier**
 - Oscillator**
 - Modulator/Demodulator**
- **Standard Cells and Memories**
 - Inverter, Switch, NAND, NOR, AOI/OAI**
 - Delay and Power Consumption**
 - ROM, SRAM, DRAM**
 - Memory Generators**
- **Digital Circuits**
 - Adders**
 - Multipliers**
- **Digital Systems**
 - General Purpose Processor**
 - Digital Signal Processor**
 - Peripherals**



Low Noise Amplifier

   

Voltage Control Oscillator

 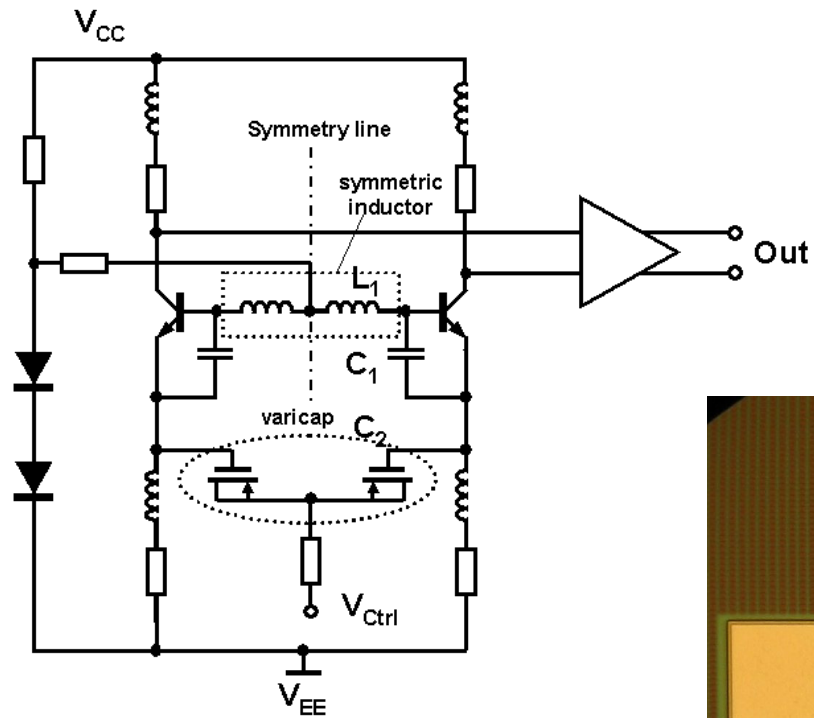

Modulator/Demodulator

  

Logic Functions

- **Function**

$f = a'b + ab'$: a is a variable, a and a' are literals, ab' is a term

- ***Irredundant* Function**

No literal can be removed without changing its value

- **Implementing logic functions is non-trivial**

No logic gates in the library for all logic expressions

A logic expression may map into gates that consume a lot of area, time, or power

- **A set of functions f_1, f_2, \dots is complete if every Boolean function can be generated by a combination of the functions from the set**

NAND and NOR are complete sets



AND and OR are not complete

Transmission gates are not complete

- **Incomplete set of logic gates**


No way to design arbitrary logic

Inverter

  


Switch

 - Complementary switch produces full-supply voltages for both logic 0 and logic 1
 n-type transistor conducts logic 0
 p-type transistor conducts logic 1




complementary

 


n-type

NAND Gate

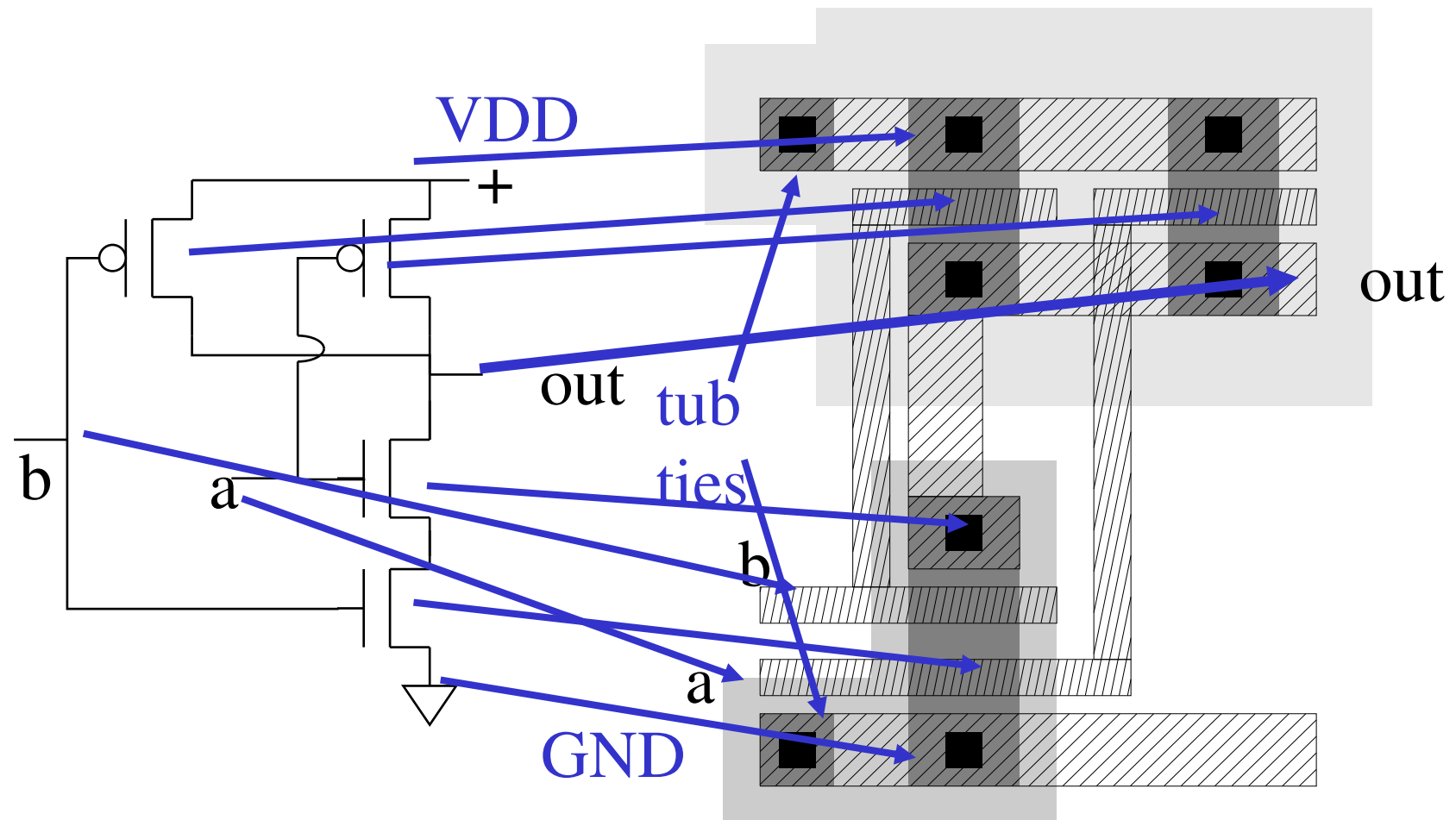

NOR Gate

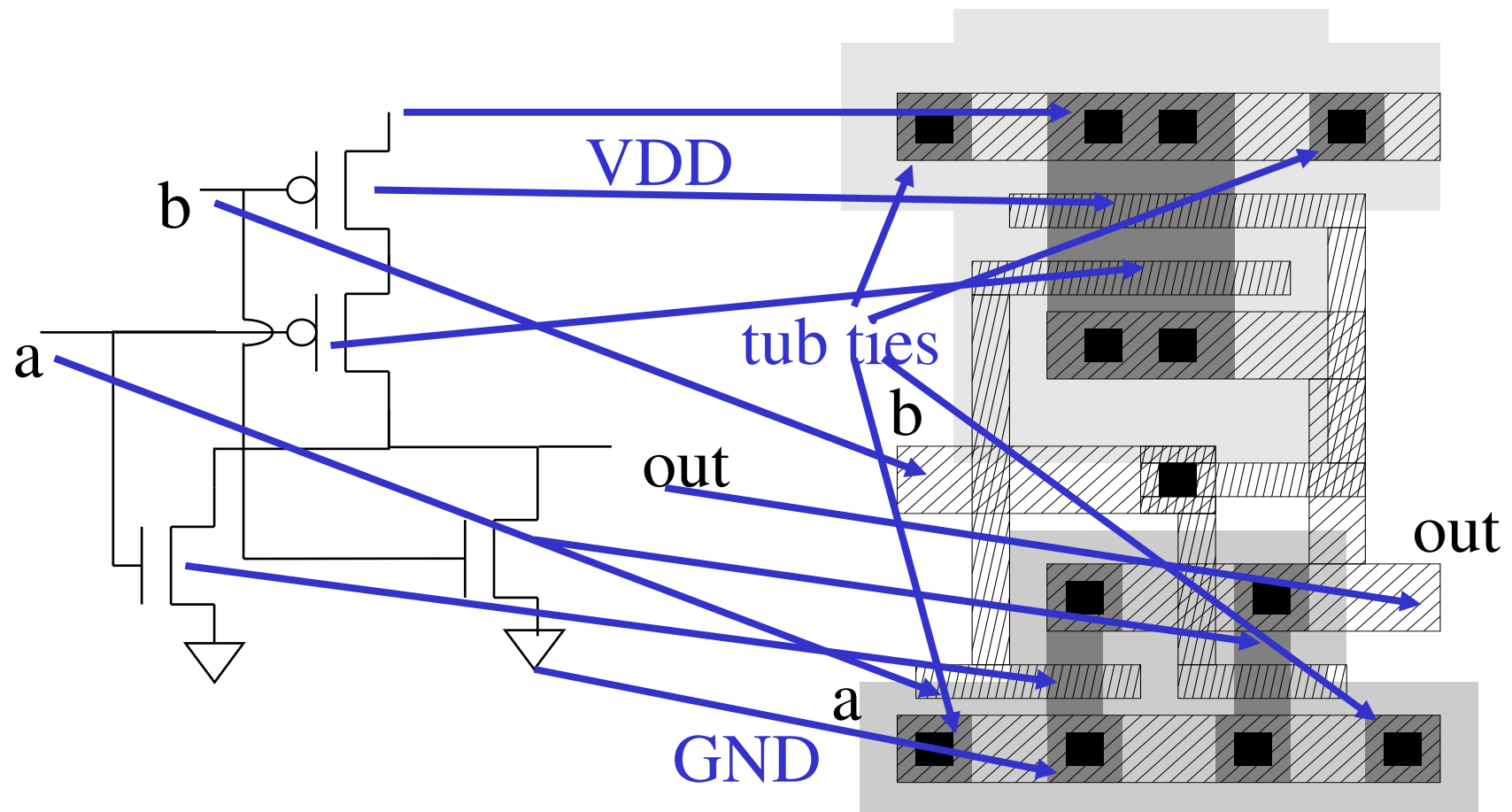

AOI/OAI Gates

- AOI = and/or/invert
- OAI = or/and/invert
- Implement larger functions
- Pull-up and pull-down networks are compact

Smaller area, higher speed than NAND/NOR network equivalents

- AOI312



And 3 inputs

And 1 input (dummy)

And 2 inputs


Or together these term

Invert

  


Logic Levels

 
- Solid logic 0/1 defined by V_{SS}/V_{DD}
- Inner bounds of logic values V_L/V_H are not directly determined by circuit properties, as in some other logic families



 - Levels at output of one gate must be sufficient to drive next gate




Inverter Transfer Curve

 

- Choose threshold voltages at points where slope of transfer curve is -1
- Inverter has
 - High gain between V_{IL} and V_{IH} points
 - Low gain at outer regions of transfer curve
- Note that logic 0 and 1 regions are not equally sized
 - In this case, high pull-up resistance leads to smaller logic 1 range
- Noise margins are $V_{DD} - V_{IH}$ and $V_{IL} - V_{SS}$
 - Noise must exceed noise margin to make second gate produce wrong output

RC Model for Delay

- **Delay**
Time required for gate's output to reach 50% of final value
- **Transition time**
Time required for gate's output to reach 10% (logic 0) or 90% (logic 1) of final value
- **Gate delay based on RC time constant**
 $V_{out}(t) = V_{DD} \exp\{-t/[(R_n+R_L)C_L]\}$
 $t_d = 0.69 R_n C_L, t_f = 2.3 R_n C_L$
- **0.5 μm process**
 $R_n = 3.9 \text{ k}\Omega, C_L = 0.68 \text{ fF}$
 $t_d = 0.69 \times 3.9 \times .68\text{E-}15 = 1.8 \text{ ps}$
 $t_f = 2.3 \times 3.9 \times .68\text{E-}15 = 6.1 \text{ ps}$
- For pull-up time, use pull-up resistance
- Current source model (in power/delay studies)
 $t_f = C_L (V_{DD}-V_{SS})/[0.5 k' (W/L) (V_{DD}-V_{SS}-V_t)^2]$
- **Fitted model**
Fit curve to measured circuit characteristics

 

Power Consumption

- Clock frequency

$$f = 1/t$$

- Energy

$$E = C_L(V_{DD} - V_{SS})^2$$

- Power

$$E \times f = f C_L(V_{DD} - V_{SS})^2$$

- Almost all power consumption comes from switching behavior

A single cycle requires one charge and one discharge of capacitor

- Static power dissipation

Comes from leakage currents


- Surprising result

Resistance of the pull-up/pull-down transistor drops out of energy calculation

Power consumption is independent of the sizes of the pull-up and pull-down transistors


- Static CMOS power-delay product is independent of frequency

Voltage scaling depends on this fact

 

Memory Architecture

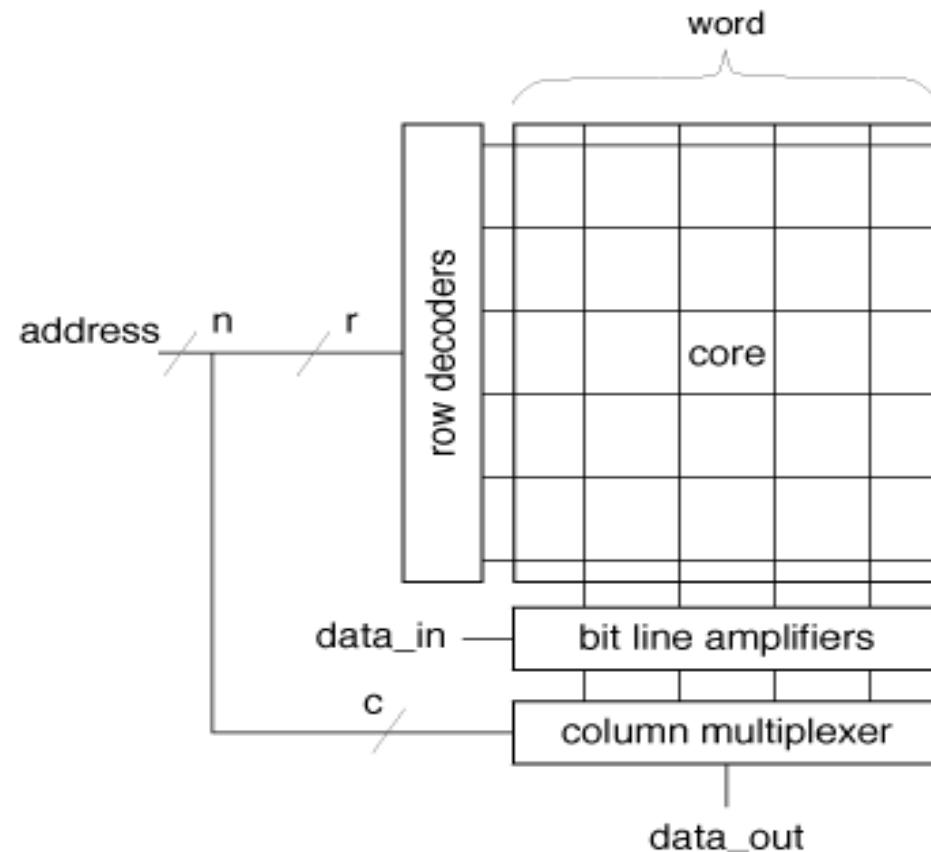- Address is divided into row and column
Row may contain full word or more than one word
- Selected row drives/senses bit lines in columns
- Amplifiers/drivers read/write bit lines




Read-Only Memory (ROM)

- ROM core is organized as an array of NOR gates



Pull-down transistors of NOR determine programming
- Erasable ROMs require special processing that is not typically available
- ROMs on digital ICs are generally mask-programmed

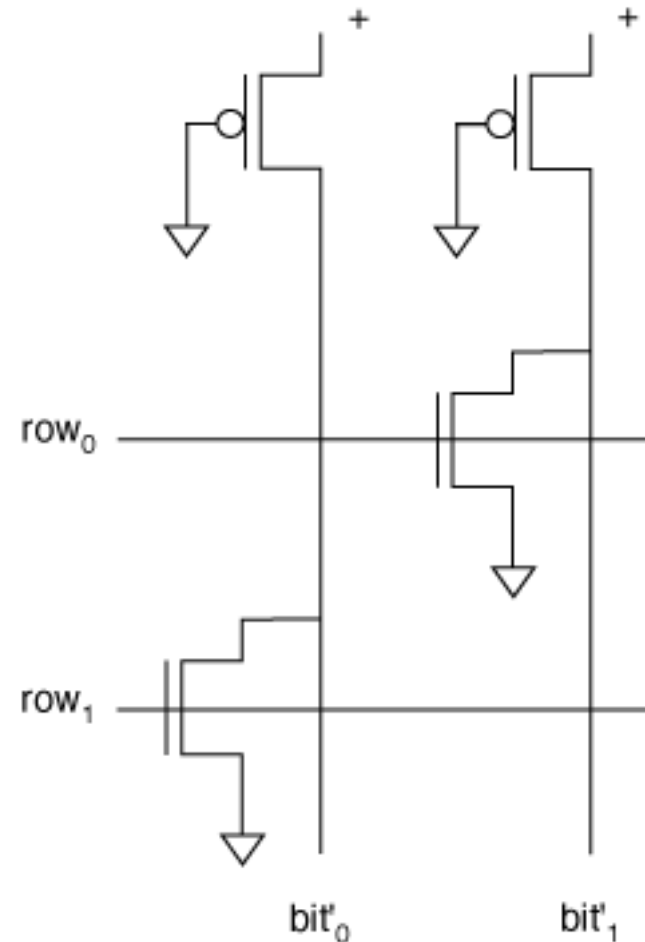Placement of pull-downs determines ROM contents




Static Random-Access Memory (SRAM)

- Core cell uses six-transistor circuit to store value
- Value is stored symmetrically
 - Both true and complement are stored on cross-coupled transistors
- SRAM retains value as long as power is applied to circuit
- Read
 - Precharge bit and bit' high
 - Set select line high from row decoder
 - One bit line will be pulled down
- Write
 - Set bit/bit' to desired (complementary) values
 - Set select line high
 - Drive on bit lines will flip state if necessary

  


SRAM Sense Amplifier

 - **Differential pair**
Takes advantage of complementarity of bit lines
- **One bit line goes low**
One arm of diff pair reduces its current, causing compensating increase in current of another arm
- **Sense amp can be cross-coupled to increase speed**



Dynamic Random-Access Memory (DRAM)

- First form of DRAM
 - Modern commercial DRAMs use one-transistor cell
- Cell can easily be made with a digital technology process
- Dynamic RAM loses value due to charge leakage
 - Must be refreshed
- Value is stored on gate capacitance of transistor t_1
- Read
 - read = 1, write = 0, read_data' is precharged
 - t_1 will pull down read_data' if 1 is stored
- Write
 - read = 0, write = 1, write_data = value
 - Guard transistor writes value onto gate capacitance

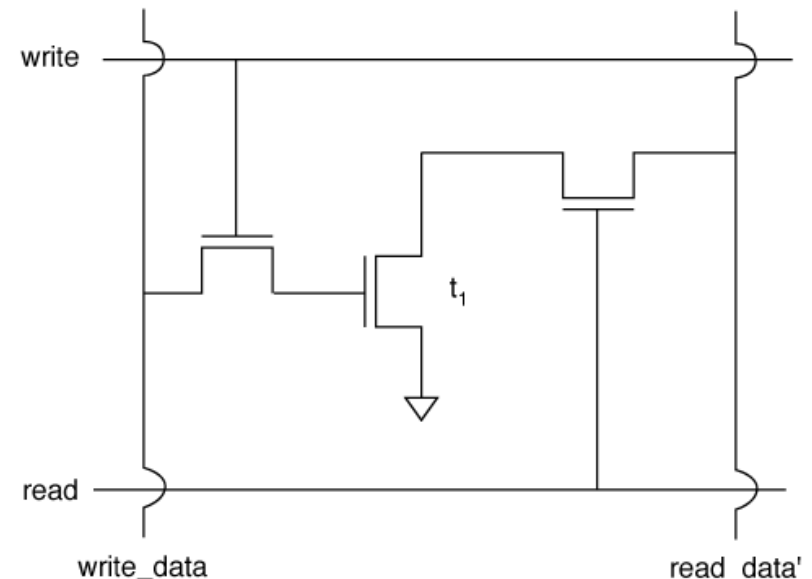

Memory Generators

- A software tool which can create memories (ROM or RAM blocks) in a range of sizes as needed

The customer usually wants a particular number of words (depth) and bits (width) for each memory ordered

Each of the final building blocks (physical layout) will be implemented as a stand-alone, densely packed, pitch-matched array

- Complex layout generators and state-of-the-art logic and circuit design techniques offer

Embedded memories of extreme density and performance

- Each memory generator is a set of various, parameterized generators

Layout generator generates an array of custom, pitch-matched leaf cells

Schematic generator and Net-lister extracts a net-list used for both layout vs. schematic and functional verification

Function and Timing model generators create models for gate level simulation, dynamic/static timing analysis and synthesis

Symbol generator generates schematic

Critical Path generator is used for both circuit design and timing characterization



Full Adder

- Computes one-bit sum and carry


$$s_i = a_i \oplus b_i \oplus c_{in}$$

$$c_{out} = a_i b_i + a_i c_{in} + b_i c_{in}$$

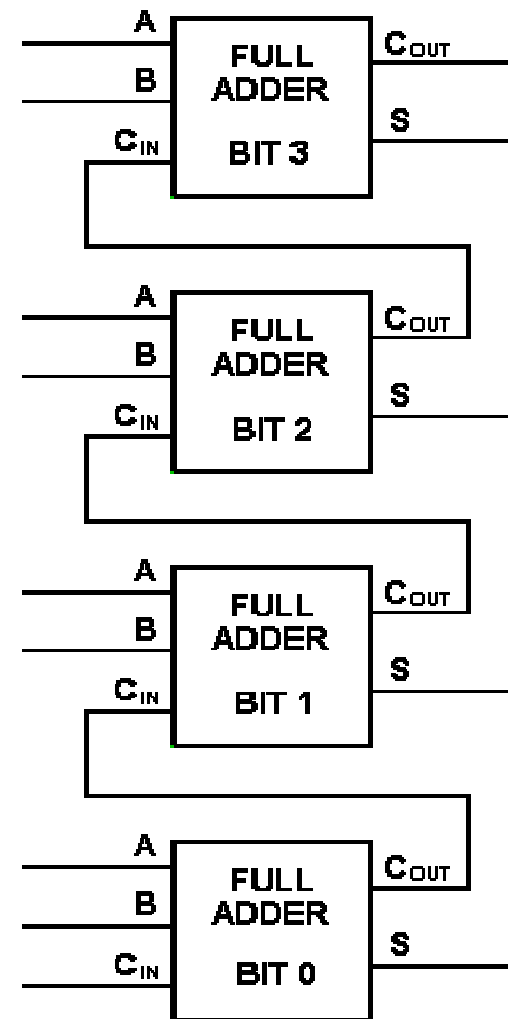 - Ripple-carry adder: n-bit adder built from full adders
- Delay of ripple-carry adder goes through all carry bits




Combinational Multiplier

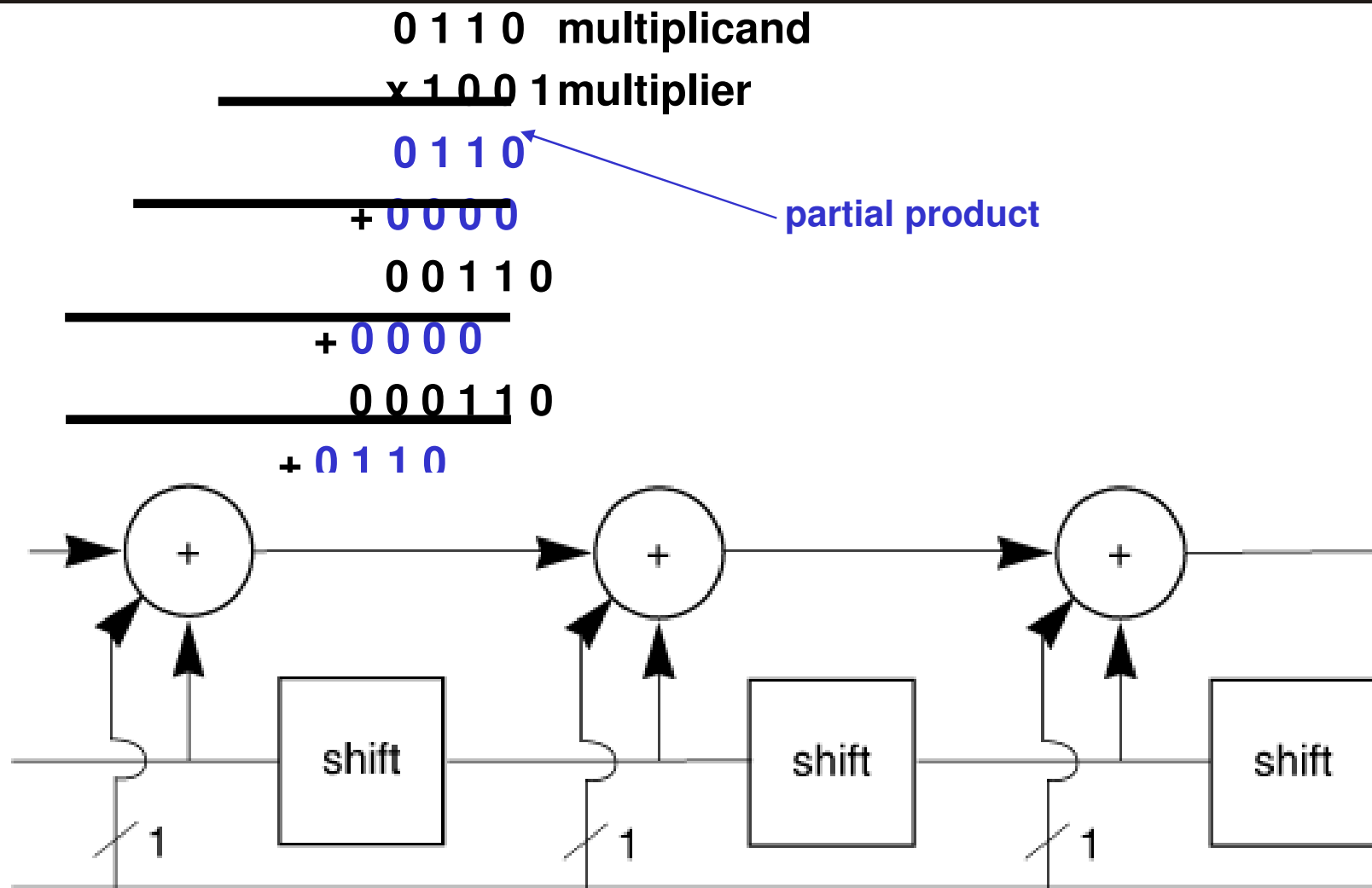


Array Multiplier

 - Array multiplier is an efficient layout of a combinatorial multiplier
- Array multipliers may be pipelined to decrease clock period at the expense of latency




Wallace Tree

 - Reduces depth of adder chain
- Built from carry-save adders
 - Three inputs a, b, c
 - Produces two outputs y, z
 - $y + z = a + b + c$
- Carry-save equations
 - $y_i = \text{parity}(a_i, b_i, c_i)$
 - $z_i = \text{majority}(a_i, b_i, c_i)$
- At each stage, i numbers are combined to form $2i/3$ sums
- Final adder completes the summation
- Wiring is more complex



Basic Processor Architecture

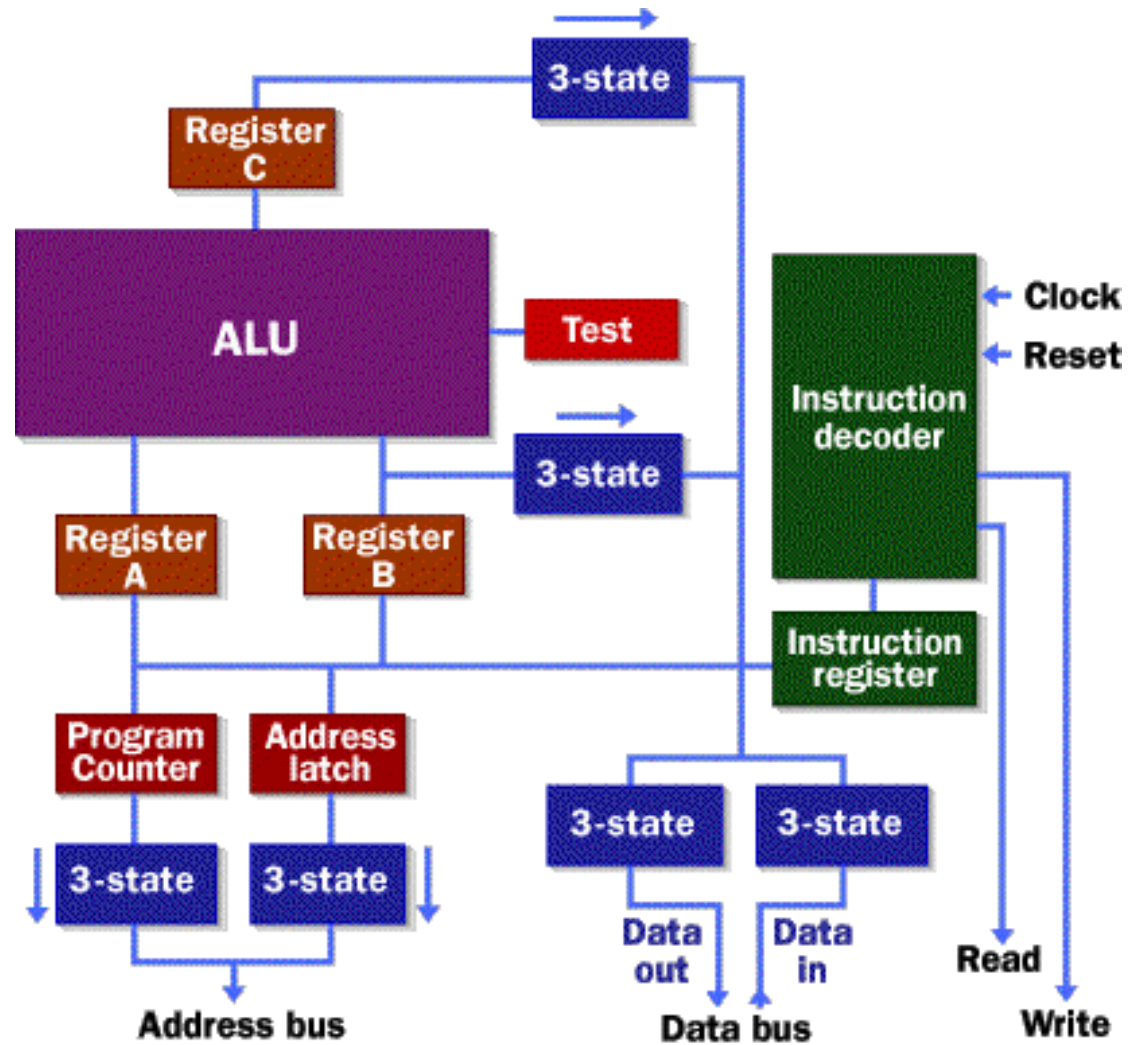

©2000 How Stuff Works

Processor Units

- Registers keep data and instructions

Registers A, B, C and the address register are made of flip-flops

The program counter is a register that can increment by 1 and reset to 0

- An ALU might add, subtract, multiply and divide n-bit numbers

The ALU could be as simple as an 8-bit adder

- The test register holds values of comparisons performed in the ALU

An instruction decoder uses these values to make decisions

- A tri-state buffer passes a 1, a 0 or disconnects its output

Multiple outputs can be connected to a wire but only one actually drives a 1 or a 0 onto the line

- The instruction register and instruction decoder are responsible for controlling all of the other components

Instruction Operators

Operator Type	Examples	
Arithmetic and Logical	Integer Operations: Add, Subtract, And, Or	
Data Transfer	Loads/Stores (Moves With Memory Addressing)	
Control	Branch, Jump, Procedure Call and Return	
System	Operating System Call, Virtual Memory Instructions	
Floating Point	Floating-point Operations: Add, Multiply	
Decimal	Decimal Operations: Add, Multiply, Decimal-to-character	
String	Move, Compare, Search	
Graphics	Pixel Operations, Compression/Decompression	

← Instructions

Total Executed on Integers		
1	Load	22%
2	Conditional Branch	20%
3	Compare	16%
4	Store	12%
5	Add	8%
6	And	6%
7	Sub	5%
8	Reg-Reg Move	4%
9	Call	1%
10	Return	1%

Percentage of Executed →

An Example: The ADD Instruction

- Instruction can be broken down as a set of sequenced operations
They manipulate the components of the processor
- During the first clock cycle, the instruction decoder needs to
Activate the tri-state buffer for the program counter
Activate the RD line
Activate the data-in tri-state buffer
Latch the instruction into the instruction register
- During the second clock cycle, the ADD instruction is decoded
Set the operation of the ALU to addition
Latch the output of the ALU into the register
- During the third clock cycle, the program counter is incremented
This could be overlapped into the second clock cycle

Pipelining

- Pipelining increases instruction throughput by breaking up the instruction into different stages

Instruction fetch (IF) - obtaining the requested instruction from memory

Instruction decode (ID) - decoding the instruction and sending out the various control lines

Execution (EX) - performing any calculations

Memory and IO (M) - storing and loading values to and from memory

Write back (WB) - writing the result of a calculation, memory access or input into the register

There are more instructions in various execution stages simultaneously




It looks like one instruction completes every clock cycle

Hazards

- **Data hazards - Instruction attempts to use the result of previous instructions not yet finished**


Stalling - Halting the instruction flow until the required result is ready to be used

   Forwarding - The result is forwarded from the EX stage of previous to the EX stage of next instruction



- **Control hazards - Changes in the normal program execution flow**
Events such as branches, interrupts and exceptions
- **Structural hazards - The hardware is unable to handle certain combinations of instructions simultaneously**

Full Processor Architecture

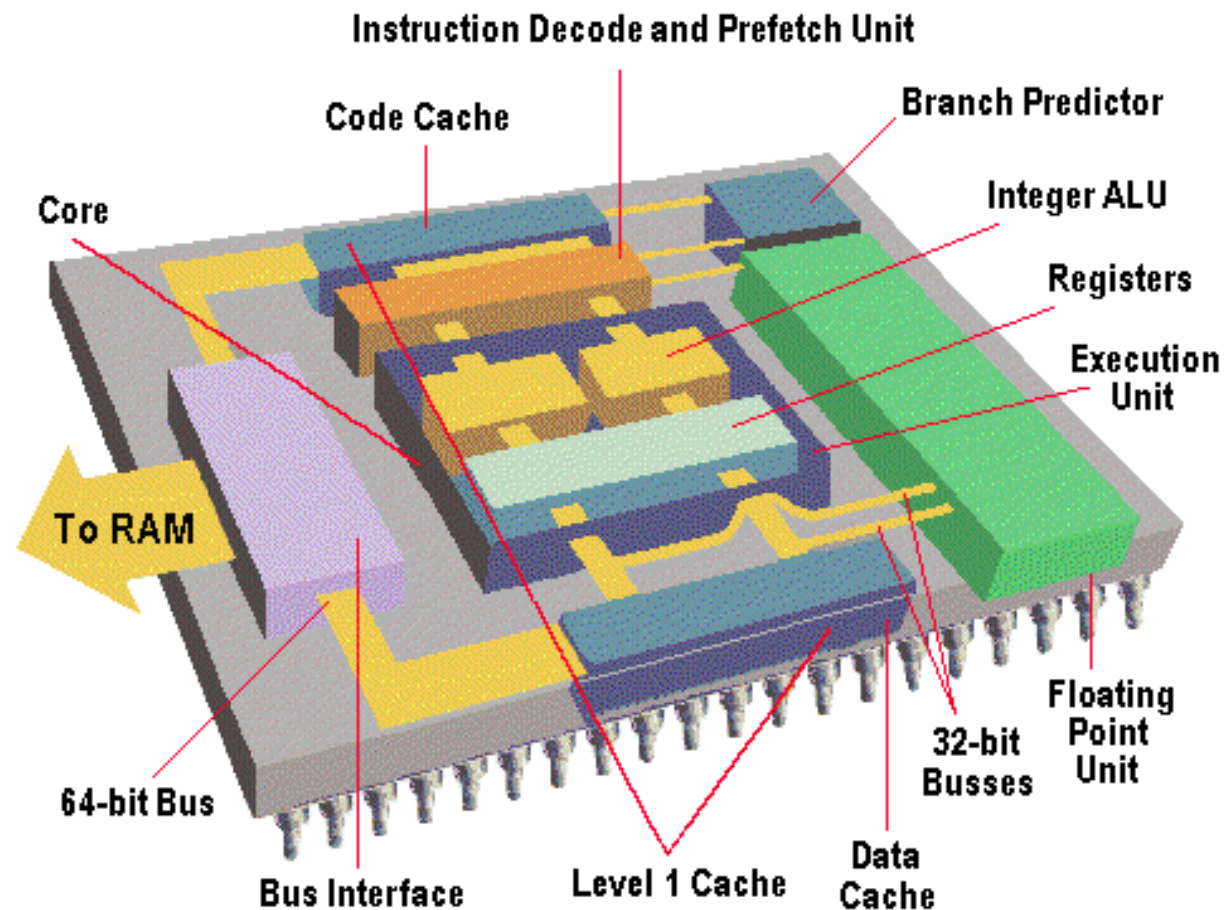

Processor Program Properties

- Programs tend to reuse already used data and instructions


A rule of thumb: A program spends 90% of its execution time in only 10% of the code

- Temporal locality


Recently used items are likely to be used in the near future

- Spatial locality

 Items with addresses near each other tend to be used close together in time



Memory Hierarchy

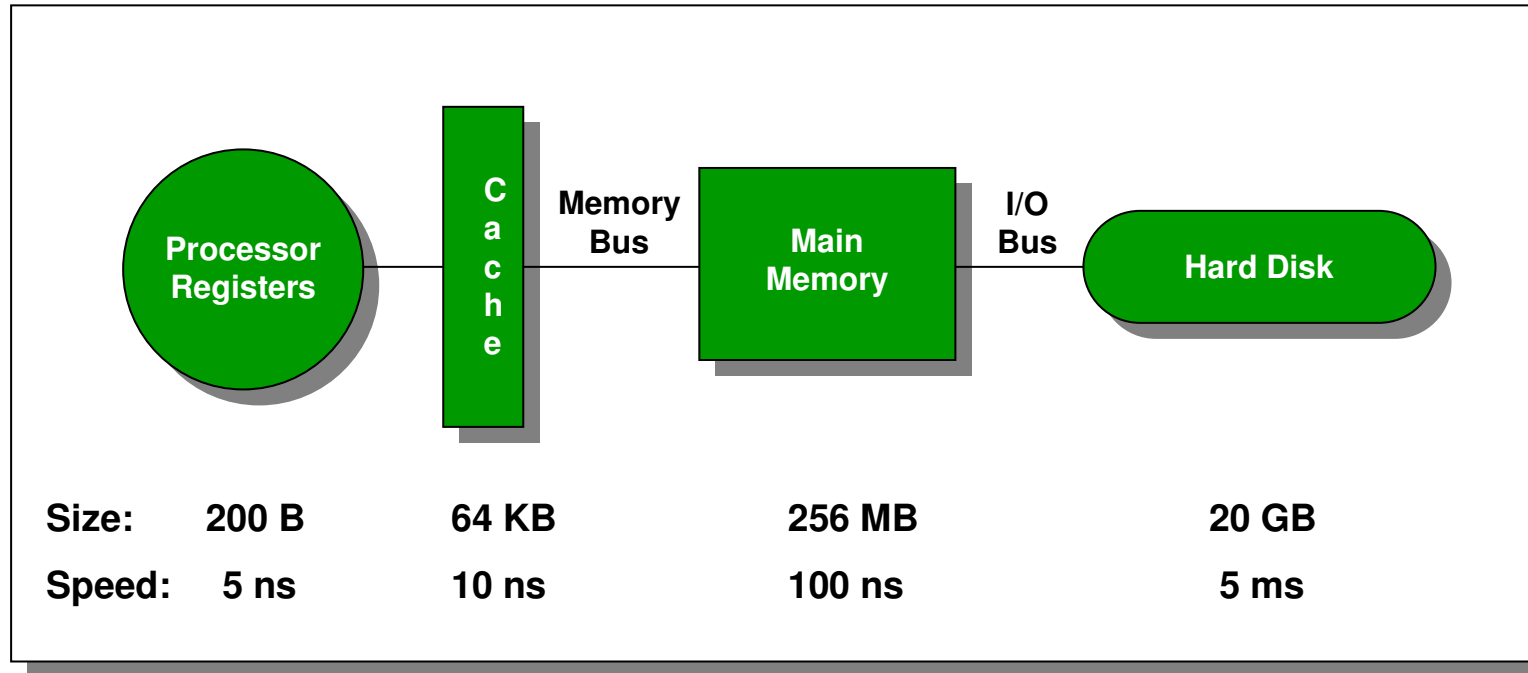

$$Speedup = \frac{1}{(1 - Fraction_{cache}) + Fraction_{cache} / Speedup_{cache}}$$

Cache Features

- A cache is a small, fast memory located close to the processor that holds the most recently accessed instructions or data

When requested data are found in the cache, it is a *cache hit*

If the access fails, a *cache miss* occurs and the request is forwarded to the main memory


- A cache is of use only if it reduces the mean access time significantly (the hit-rate must be high)

The hit-rate can be further increased by pre-fetch mechanisms

- After the process change, the cache hit-rate is small (cold cache)

The cache warm-up time has to be taken into account for task switching

Cache Organization

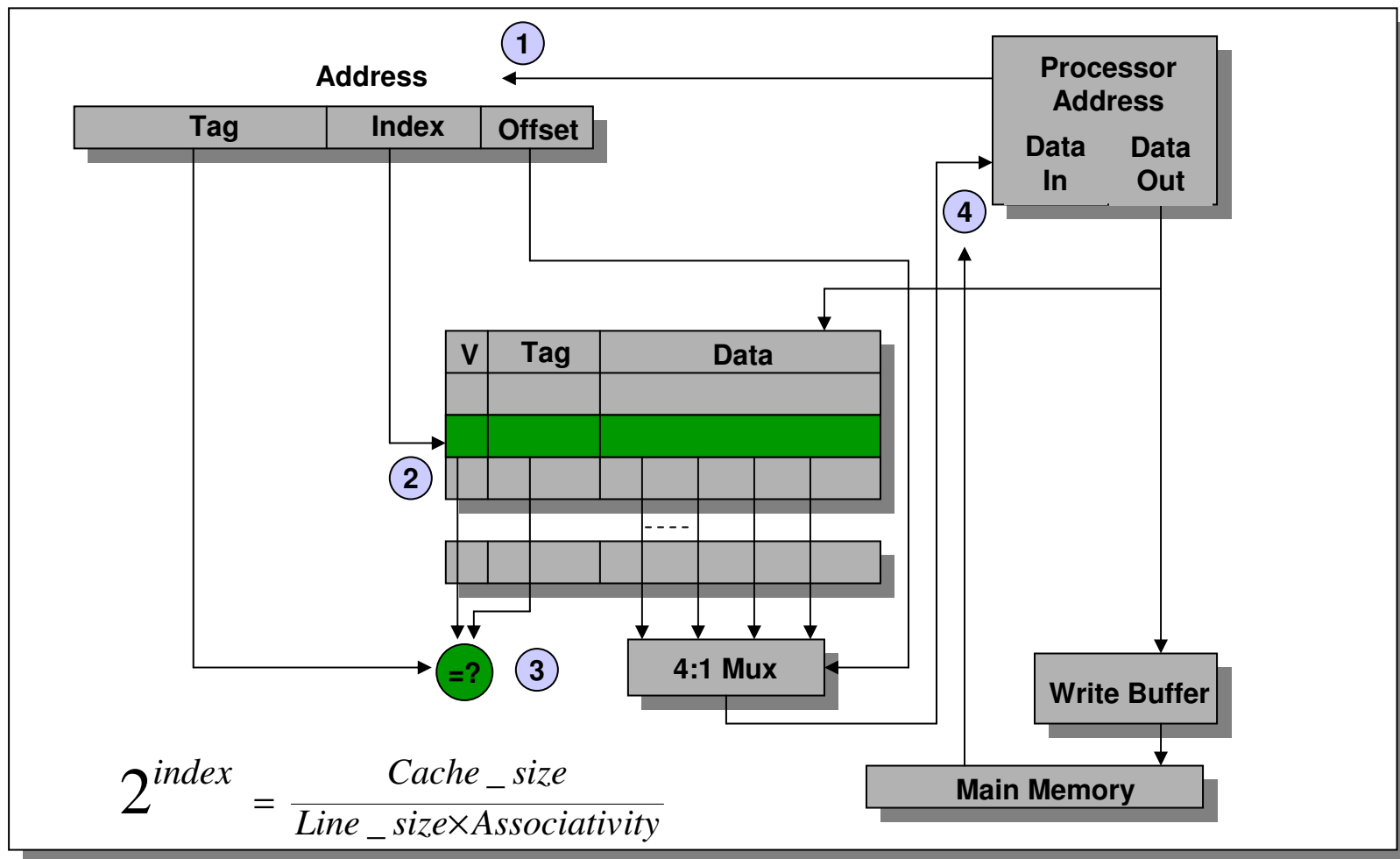

Cache Addressing

- A 16 KB cache memory with a 16-byte cache line has 1024 cache lines

A system with 16 MB of main memory has 1024 different 16-byte lines of memory that must share a cache line

- To address 16 MB of memory, 24 address lines are needed (2^{24} is 16 M), but 16 KB only requires 14 address lines


The 10 lines of difference (since 1024 is 2^{10}) represent an index

The index selects one of the 1024 different addresses that can use a given cache line

- No matter how fast the data RAM is, the tag RAM must be slightly faster

Tag RAM access time has to be less than half of the clock cycle


Cache Associativity

 

Fully Associative Cache
Best Hit Ratio, Moderate Search Speed

Direct Mapped Cache
Good Hit Ratio, Best Search Speed

General Purpose Processor

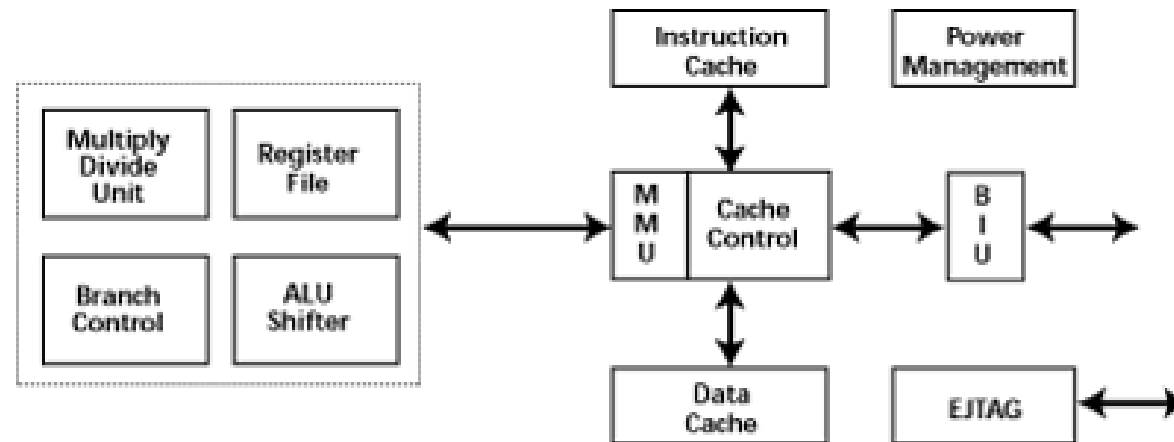

Technology	Area (mm ²) (8K I-cache and 8K D-cache)	Power/Frequency (mW/MHz)	Max Frequency (MHz)
0.25 μm	12	2.0	150
0.18 μm	4.7	1.7	260
0.13 μm	1.5	0.45	340

DSP versus GPP

- **Digital Signal Processor**

Designed to run *one program*

Recent DSPs have instruction caches but *no data caches*

Specialized complex instructions

Specialized hardware performs all key *arithmetic operations in 1 cycle*

Hardware support for managing numeric fidelity

Dedicated address generation unit

- **General Purpose Processor**

Designed to run *many programs*

May have *caches*

Simple instructions

Multiplies take *more than 1 cycle*

Shifts take *more than 1 cycle*

Other operations (saturation, rounding...) typically take *multiple cycles*

No separate address generation unit


Basics of DSPs

- **DSPs can have different data word sizes**
Word size affects precision of fixed point numbers
- **Speed defined by speed of Multiply-Accumulate (MAC) operations**
A DSP should keep the multipliers busy 100% of the time
- **Floating Point versus Fixed Point DSPs**
More expensive (2-4 times)
Much slower
- **Basic DSP algorithms**
Infinite Impulse Response (IIR) Filters
Finite Impulse Response (FIR) Filters
Fast Fourier Transformers (FFT)
Convolvers
Turbo Decoders

VLIW DSPs


- **VLIW stands for Very Long Instruction Word**
 - Multiple independent instructions per cycle**
 - Packed into single large "instruction word"**
 - May be positional, or**
 - May include routing information within sub-instructions**
- **Large complement of independent execution units**
- **More regular, orthogonal, RISC-like instructions**
 - Usually wider than typical DSP instructions**
 - Usually simpler than typical DSP instructions**
- **Large, uniform register sets**
- **Wide program and data buses**

Texas Instruments TMS320C62

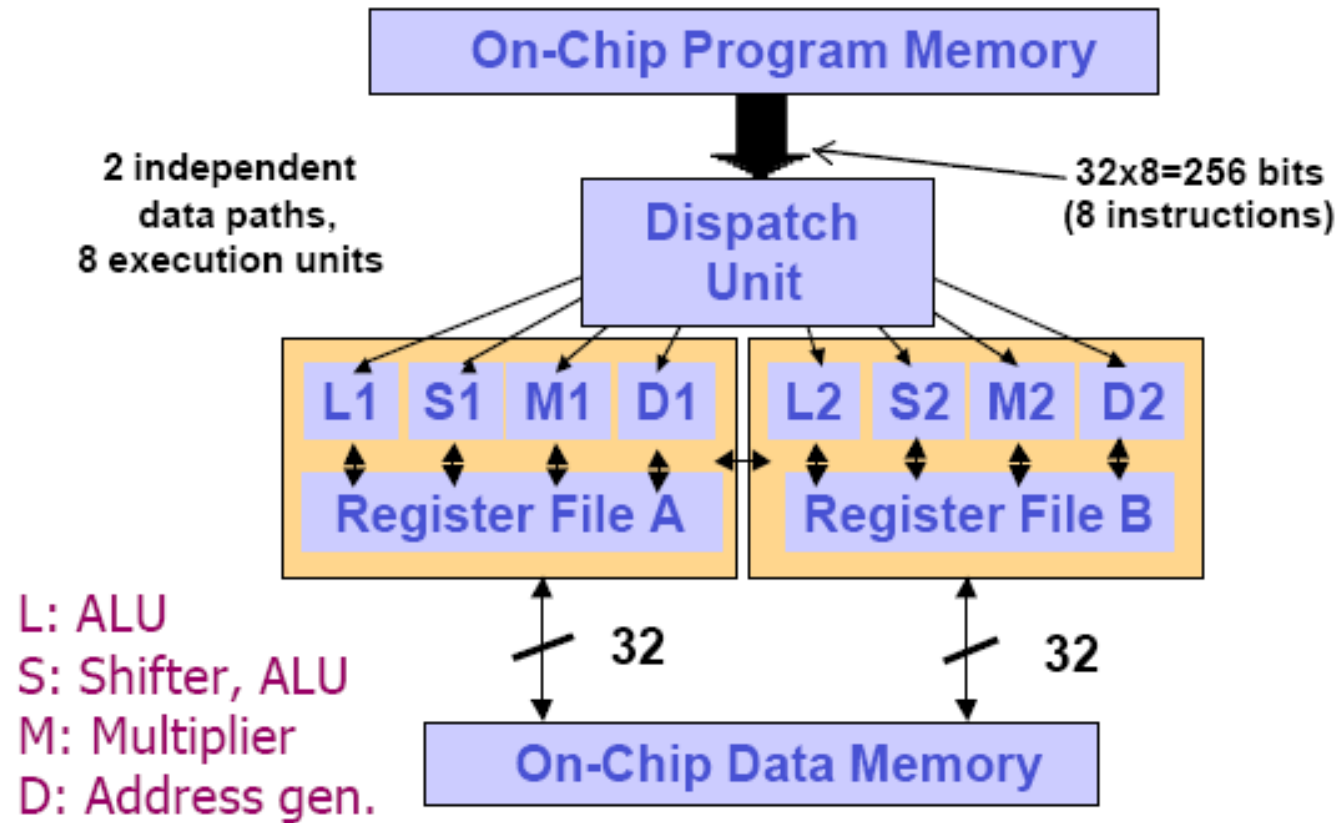


Analog Devices TigerSHARC

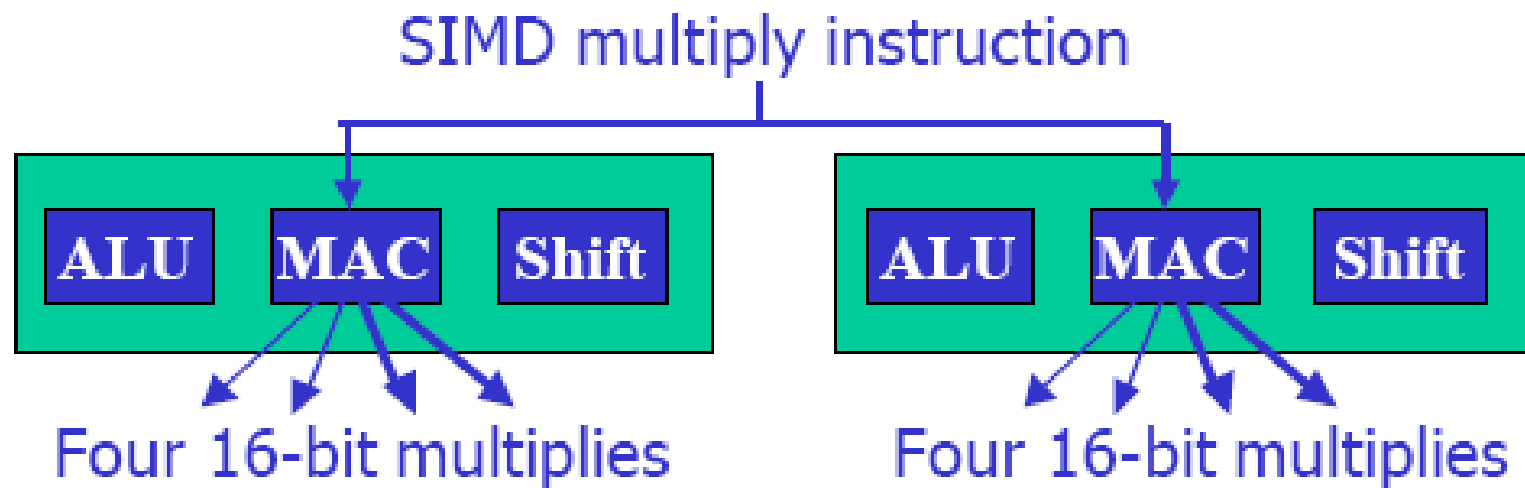- 8-bit, 16-bit, 32-bit fixed point
- 32-bit floating point
- Single instruction, multiple data
- Executes up to four instructions per cycle
- Uses 32-bit instructions




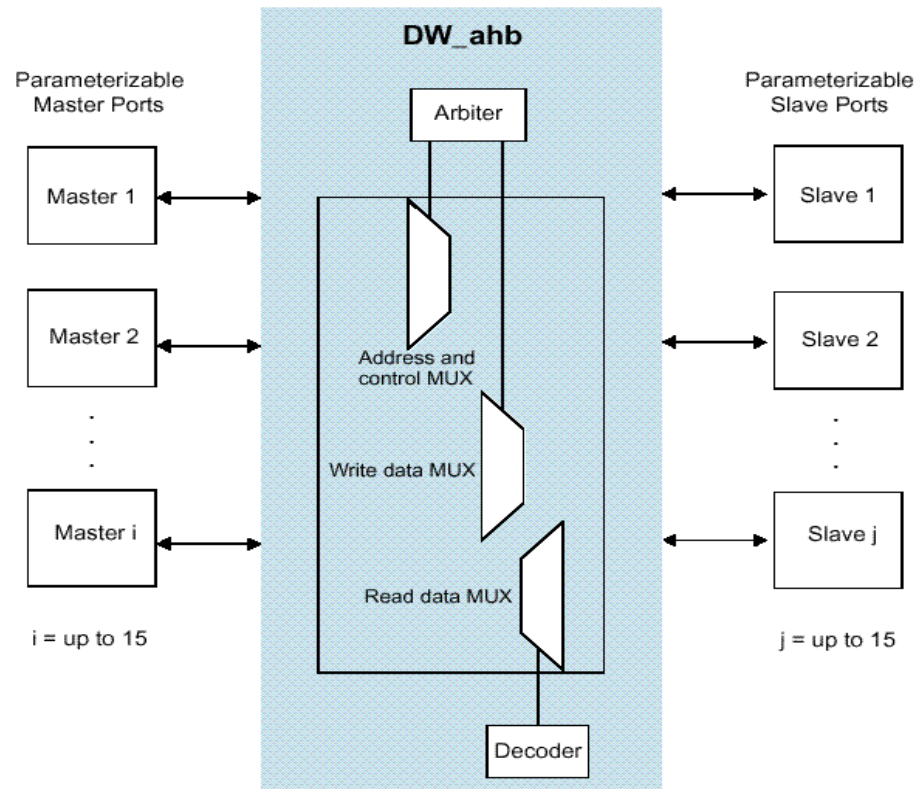Advanced Microcontroller Bus Architecture




Advanced High-performance Bus (AHB)

Advanced Peripheral Bus (APB)

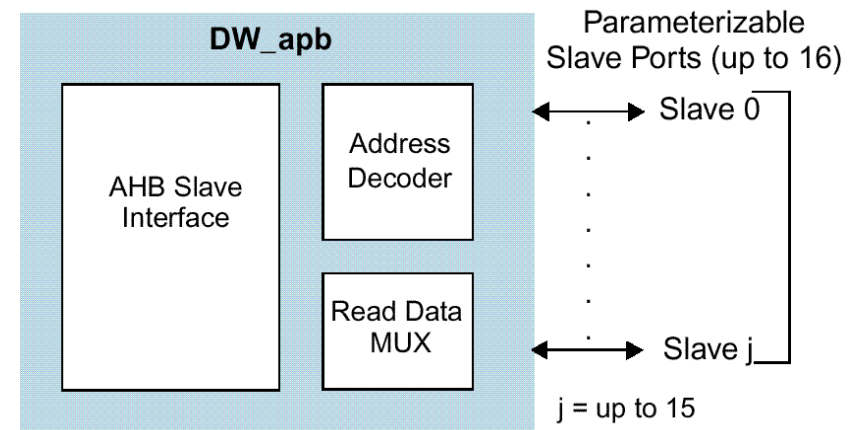


Inter-IC Bus

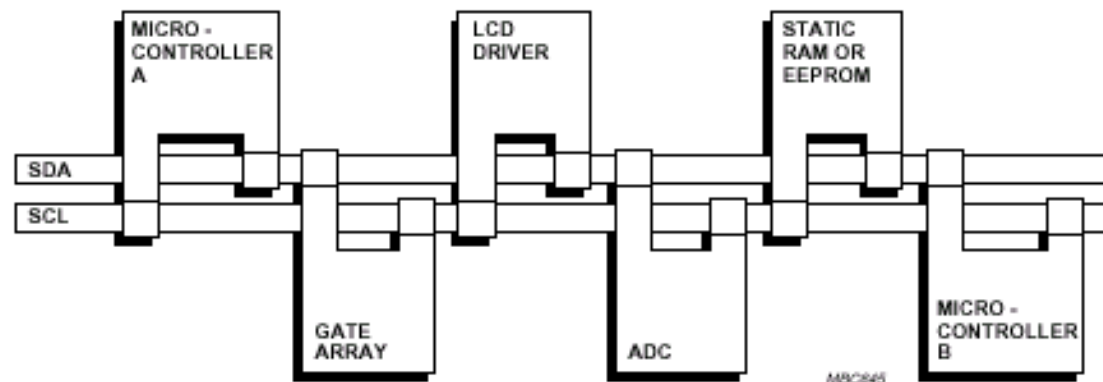- I²C bus has two wires
 - Serial data (SDA)
 - Serial clock (SCL)
- A multi-master bus
 - More than one device with the controlling capability
- I²C interface
 - Recognized by a unique address of 7 or 10 bits
 - Operates as either receiver only device or transmitter




Memory Controller

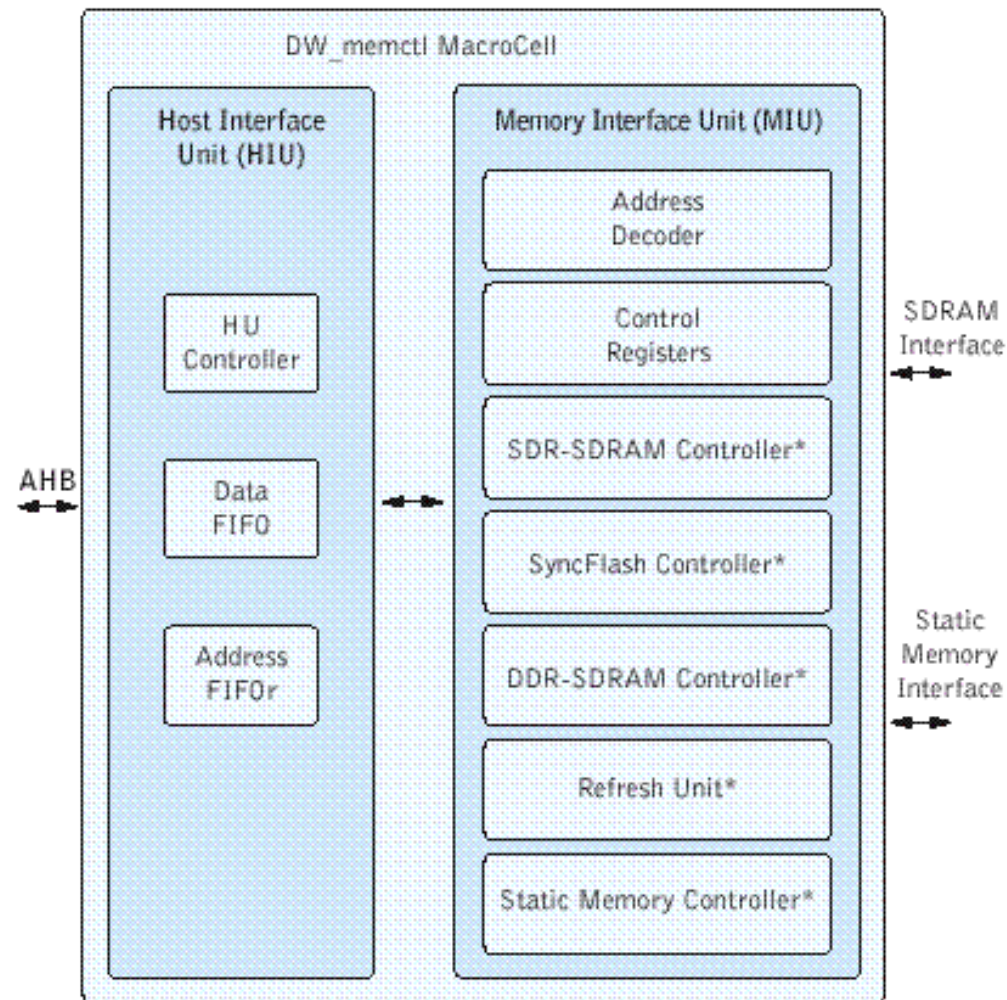


Note: *Conditional Instantiations

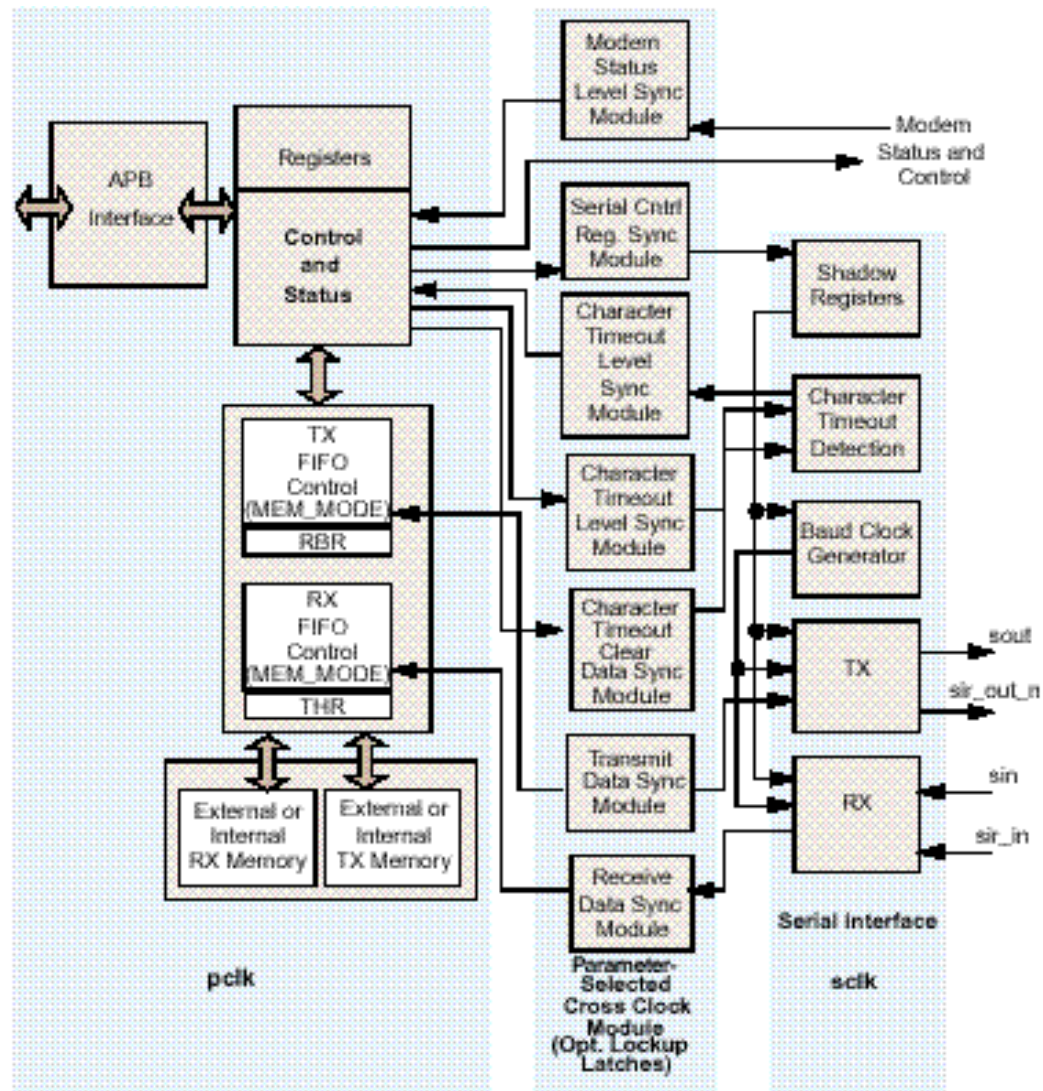Universal Asynchronous Receiver and Transmitter



General Purpose Input/Output

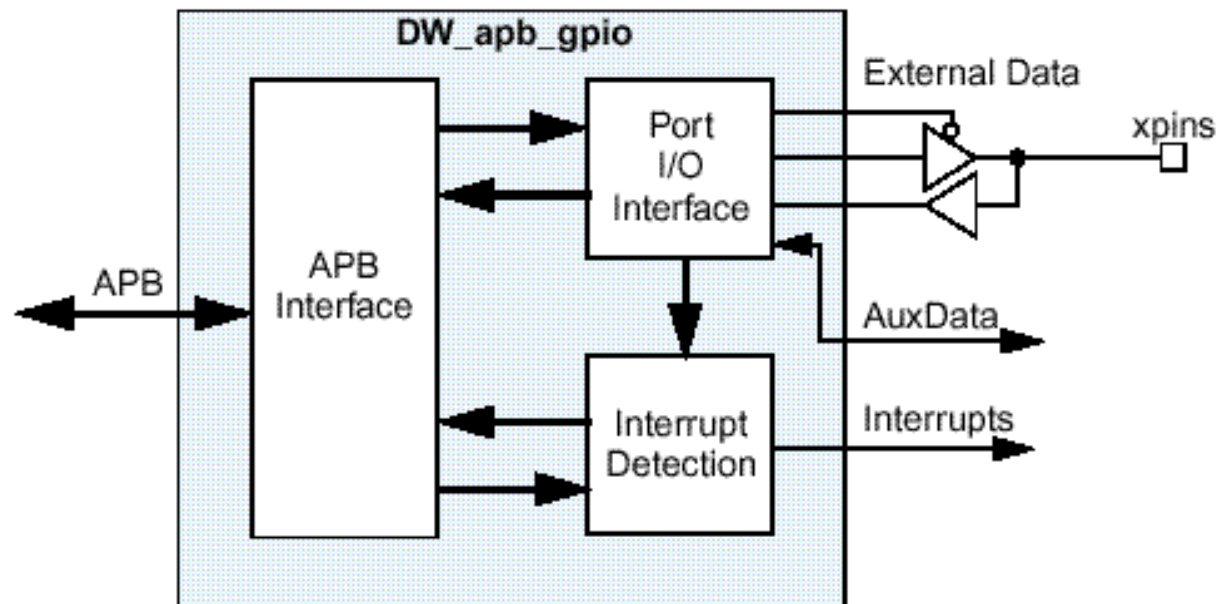

JTAG Debug Link

